

The P1-eXtreme Options Guide

08.06.23

Hours of fun and frustration with your AX84 amp.

WARNING! - Please Read this Information Carefully:

The project described in these pages utilizes **POTENTIALLY FATAL HIGH VOLTAGES**. If you are in any way unfamiliar with high voltage circuits or are uncomfortable working around high voltages, **PLEASE DO NOT RISK YOUR LIFE BY BUILDING THEM**. Seek help from a competent technician before building any unfamiliar electronics circuit. While efforts are made to ensure accuracy of these circuits, no guarantee is provided, of any kind!

USE AT YOUR OWN RISK: THE WEBMASTER, PROJECT COORDINATOR, PROJECT CONTRIBUTORS AND WEB SPACE PROVIDER EXPRESSLY DISCLAIM ALL LIABILITY FOR INJURY OR PROPERTY DAMAGE RESULTING FROM THIS INFORMATION! ALL INFORMATION IS PROVIDED 'AS-IS' AND WITHOUT WARRANTY OF ANY KIND.

COPYRIGHT AND INTELLECTUAL PROPERTY NOTICE:


The content of this document is protected by the copyright laws of the United States of America and the international copyright laws and agreements.

Except where specifically noted, Cliff Chappell or Chris Hurley owns (or has permission to use) all intellectual property rights in relation to this document and its content (including, but not limited to, all trademarks and copyright).

No part of the document may be reproduced, displayed, copied, translated, adapted, downloaded, broadcast, used or republished in any form including (without limitation) distribution, or storage in a system for retrieval.

The Variable Cathode Bias Option

This is a modification that can be made to cathode biased amps like the P1, High Octane, P1 eXtreme, and the SEL. In fact, I make this mod to all of the SE amps I build. By adding one 1K Linear potentiometer, one 1R – 0.1% resistor, two multi-meter probe test points, changing the existing cathode resistor to a 100R/5W unit, and adding a little wire, you can give yourself the ability to dial in the bias setting you want for any output tube you care to use.

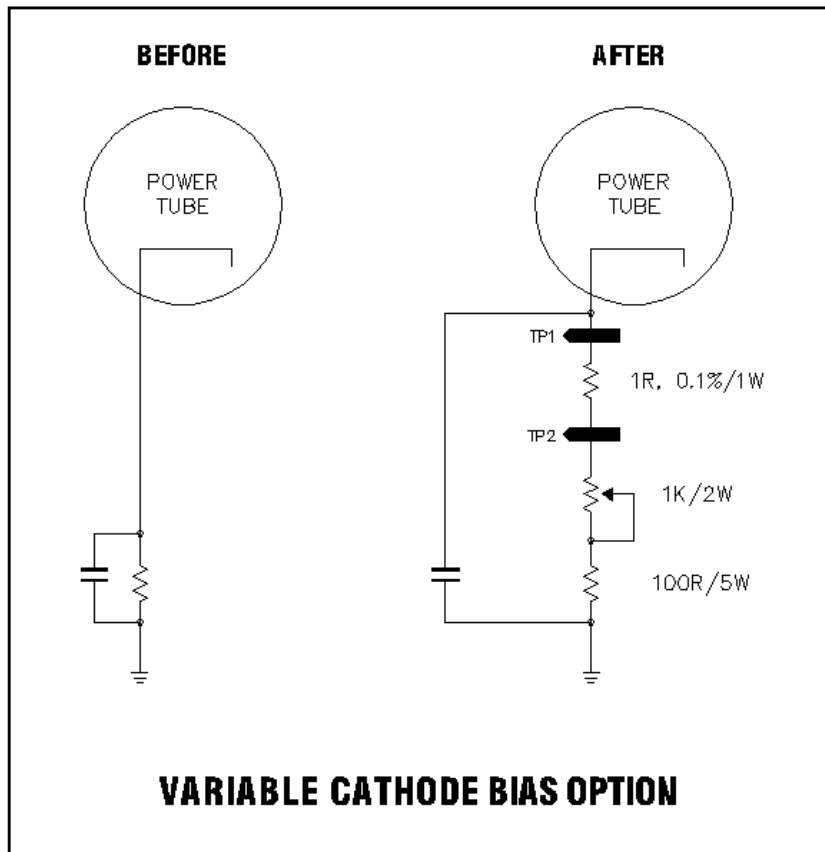

NOTE: The 100R/5W resistor should be increased to 200R/5W if you plan on using a KT88 in the amp.

The 0.1% 1R resistor (you can use a 1% resistor, but the more accurate your resistor, the more accurate your reading), is placed between the two test points. You will use your multi-meter, set to mV, to measure the voltage across the 1R resistor. Since the resistor is 1R, $V = \text{mA}$ of current that the tube is drawing.

To set the bias, first insert the positive probe in TP1 and the negative in TP2, and change the dial to mV. Pay attention to the meter. When you dial the pot one way, current (mV) increases. When you dial it the other way, current (mV) decreases. Dial the pot so that the mV reading is as low as it will go.

Now, take a reading of the anode (aka plate) voltage and use the following formula to determine the bias setting for the tube you are using: $(\text{PaMax} * 0.9) / V_a$

PaMax is the maximum plate dissipation of the tube you are using and V_a is the voltage at the anode that you measured. Once you have that number, you simply adjust the bias pot until you see that number on the display.